

BBM233 Logic Design Lab

2024 Fall

Board Experiment 1 Report

Yigitcan Kizil, 2220356084

October 11, 2024

1. Question 1

T	A	F	Dispense Food
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Figure 1: Truth Table

2. Question 2

$$F(T, A, F) = m_3 + m_6 + m_7 = \sum(3, 6, 7)$$

$$F(T, A, F) = T'AF + TAF' + TAF$$

3. Question 3

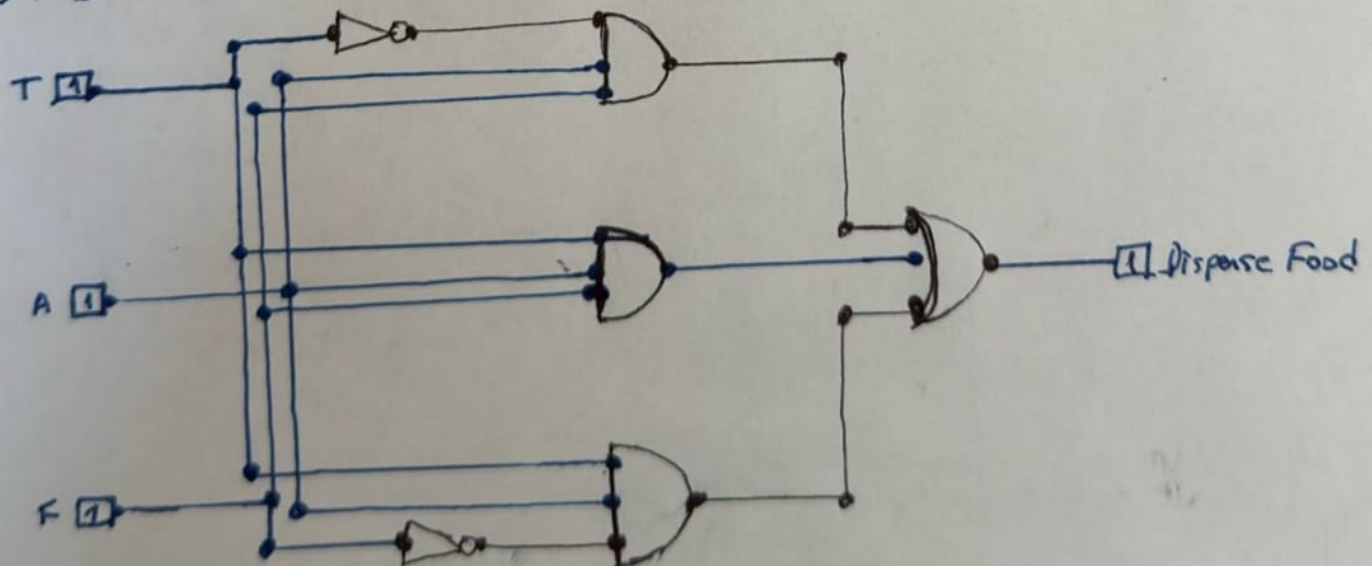


Figure 2: Circuit

4. References

- Digital Design and Computer Architecture, 2nd Edition, David Money Harris and Sarah L. Harris

Discrete Time	F	A	T
0	0	0	0
0	1	0	0
0	0	1	0
1	1	1	0
0	0	0	1
0	1	0	1
1	0	1	1
1	1	1	1

Yigitcan Kizil
2220356086

$$F(A, T) = T + AT + AT = (T, A, T) F$$

